

Contents at a Glance

Introduction	1
Part 1: Fathoming the Fundamentals of Electronics	5
CHAPTER 1: Introducing You to Electronics	7
CHAPTER 2: Gearing Up to Explore Electronics	27
CHAPTER 3: Running Around in Circuits	37
CHAPTER 4: Making Connections	53
Part 2: Controlling Current with Components	71
CHAPTER 5: Meeting Up with Resistance	73
CHAPTER 6: Obeying Ohm's Law	95
CHAPTER 7: Getting Charged Up about Capacitors	111
CHAPTER 8: Identifying with Inductors	137
CHAPTER 9: Diving into Diodes	155
CHAPTER 10: Tremendously Talented Transistors	171
CHAPTER 11: Innovating with Integrated Circuits	191
CHAPTER 12: Acquiring Additional Parts	223
Part 3: Getting Serious about Electronics	245
CHAPTER 13: Preparing Your Lab and Ensuring Your Safety	247
CHAPTER 14: Interpreting Schematics	273
CHAPTER 15: Building Circuits	293
CHAPTER 16: Mastering Your Multimeter to Measure Circuits	315
CHAPTER 17: Putting Projects Together	339
Part 4: The Part of Tens	365
CHAPTER 18: Ten Ways to Explore Electronics Further	367
CHAPTER 19: Ten Great Electronics Parts Sources	373
Glossary	379
Index	389

Table of Contents

INTRODUCTION	1
About This Book	1
Foolish Assumptions	2
Icons Used in This Book	3
Beyond the Book	3
Where to Go from Here	4
 PART 1: FATHOMING THE FUNDAMENTALS OF ELECTRONICS	 5
CHAPTER 1: Introducing You to Electronics	7
Just What Is Electronics?	8
Checking Out Electric Current	9
Exploring an atom	9
Getting a charge out of protons and electrons	11
Identifying conductors and insulators	11
Mobilizing electrons to create current	12
Understanding Voltage	13
Let the force be with you	14
Why voltage needs to be different	14
Putting Electrical Energy to Work	15
Tapping into electrical energy	15
Working electrons deliver power	16
Using Circuits to Make Sure Electrons Arrive at Their Destination	17
Supplying Electrical Energy	18
Getting direct current from a battery	19
Using alternating current from a power plant	20
Transforming light into electricity	21
Using symbols to represent energy sources	22
Marveling at What Electrons Can Do	23
Creating good vibrations	23
Seeing is believing	23
Sensing and alarming	24
Controlling motion	24
Computing	24
Voice, video, and data communications	25
 CHAPTER 2: Gearing Up to Explore Electronics	 27
Getting the Tools You Need	28
Stocking Up on Essential Supplies	31
Getting Ready to Rumble	35
Using a Solderless Breadboard	35

CHAPTER 3:	Running Around in Circuits	37
	Comparing Closed, Open, and Short Circuits	38
	Understanding Conventional Current Flow	40
	Examining a Basic Circuit	41
	Building the basic LED circuit	42
	Examining voltages	44
	Measuring current	49
	Calculating power	50
CHAPTER 4:	Making Connections	53
	Creating Series and Parallel Circuits	53
	Series connections	54
	Parallel connections	56
	Switching Electric Current On and Off	59
	Controlling the action of a switch	60
	Making the right contacts	61
	Creating a Combination Circuit	62
	Switching On the Power	66
	What Do Circuits Look Like?	67
	PART 2: CONTROLLING CURRENT WITH COMPONENTS	71
CHAPTER 5:	Meeting Up with Resistance	73
	Resisting the Flow of Current	74
	Resistors: Passive Yet Powerful	75
	What are resistors used for?	76
	Choosing a type of resistor: Fixed or variable	80
	Reading into fixed resistors	82
	Rating resistors according to power	86
	Combining Resistors	88
	Resistors in series	89
	Resistors in parallel	91
	Combining series and parallel resistors	93
CHAPTER 6:	Obeying Ohm's Law	95
	Defining Ohm's Law	95
	Driving current through a resistance	95
	It's constantly proportional!	96
	One law, three equations	97
	Using Ohm's Law to Analyze Circuits	98
	Calculating current through a component	98
	Calculating voltage across a component	99
	Calculating an unknown resistance	101

Seeing Is Believing: Ohm's Law Really Works!	102
What Is Ohm's Law Really Good For?	105
Analyzing complex circuits.	105
Designing and altering circuits	107
The Power of Joule's Law	109
Using Joule's Law to choose components	109
Joule and Ohm: perfect together	110
CHAPTER 7: Getting Charged Up about Capacitors	111
Capacitors: Reservoirs for Electrical Energy	112
Charging and Discharging Capacitors	113
Watching a capacitor charge	115
Opposing voltage change.	118
Giving alternating current a pass	119
Discovering Uses for Capacitors	120
Characterizing Capacitors	121
Defining capacitance.	121
Keeping an eye on the working voltage	123
Choosing the right dielectric for the job.	123
Sizing up capacitor packaging	124
Being positive about capacitor polarity	124
Reading into capacitor values	125
Varying capacitance.	127
Interpreting capacitor symbols	128
Combining Capacitors.	128
Capacitors in parallel	128
Capacitors in series.	129
Teaming Up with Resistors.	130
Timing is everything	130
Calculating RC time constants	132
Varying the RC time constant.	133
CHAPTER 8: Identifying with Inductors	137
Kissing Cousins: Magnetism and Electricity.	138
Drawing the (flux) lines with magnets	138
Producing a magnetic field with electricity	139
Inducing current with a magnet	140
Introducing the Inductor: A Coil with a Magnetic Personality.	141
Measuring inductance	142
Opposing current changes.	142
Calculating the RL time constant.	144
Keeping up with alternating current (or not!)	144
Behaving differently depending on frequency	144
Uses for Inductors.	145

Using Inductors in Circuits	146
Reading inductance values.	147
Combining shielded inductors.	147
Tuning in to Radio Broadcasts.	148
Resonating with RLC circuits	148
Ensuring rock-solid resonance with crystals	150
Influencing the Coil Next Door: Transformers	151
Letting unshielded coils interact	151
Isolating circuits from a power source.	152
Stepping up, stepping down voltages.	152
CHAPTER 9: Diving into Diodes	155
Are We Conducting or Aren't We?	155
Sizing up semiconductors	156
Creating N-types and P-types	157
Joining N-types and P-types to create components.	157
Forming a Junction Diode.	158
Biasing the diode.	159
Conducting current through a diode	160
Rating your diode	161
Identifying with diodes	161
Which end is up?	162
Using Diodes in Circuits	162
Rectifying AC.	162
Regulating voltage with Zener diodes	164
Seeing the light with LEDs	165
Turning on an LED.	167
Other uses of diodes.	170
CHAPTER 10: Tremendously Talented Transistors	171
Transistors: Masters of Switching and Amplifying	172
Bipolar junction transistors	173
Field-effect transistors	174
Recognizing a transistor when you see one	175
Making all kinds of components possible	176
Examining How Transistors Work.	176
Using a model to understand transistors	178
Operating a transistor.	179
Amplifying Signals with a Transistor.	180
Biasing the transistor so it acts like an amplifier	182
Controlling the voltage gain.	182
Configuring transistor amplifier circuits	183
Switching Signals with a Transistor.	184
Choosing Transistors	184
Important transistor ratings	185
Identifying transistors.	186

Gaining Experience with Transistors	186
Amplifying current	186
The switch is on!	189
CHAPTER 11: Innovating with Integrated Circuits	191
Why ICs?	192
Linear, Digital, or Combination Plate?	193
Making Decisions with Logic	194
Beginning with bits	194
Processing data with gates.	196
Simplifying gates with truth tables	199
Creating logical components	199
Using ICs	202
Identifying ICs with part numbers.	202
Packaging is everything	202
Probing IC pinouts	205
Relying on IC datasheets	206
Using Your Logic	207
Seeing the light at the end of the NAND gate	208
Turning three NAND gates into an OR gate.	209
Hanging Out with Some Popular ICs	211
Operational amplifiers	211
IC time machine: the 555 timer	213
Counting on the 4017 decade counter.	220
Microcontrollers	221
Other popular ICs	222
CHAPTER 12: Acquiring Additional Parts	223
Making Connections	224
Choosing wires wisely	224
Plugging in to connectors	226
Powering Up	228
Turning on the juice with batteries	228
Getting power from the sun	232
Using wall power to supply higher DC current or voltage (not recommended)	232
Using Your Sensors	235
Seeing the light	235
Capturing sound with microphones	236
Feeling the heat	238
More energizing input transducers	238
Experiencing the Outcome of Electronics	239
Speaking of speakers	240
Sounding off with buzzers	241
Creating good vibrations with DC motors	242

PART 3: GETTING SERIOUS ABOUT ELECTRONICS 245

CHAPTER 13: Preparing Your Lab and Ensuring Your Safety 247

Picking a Place to Practice Electronics	248
The top ingredients for a great lab	248
Workbench basics	249
Acquiring Tools and Supplies.	250
Amassing a multimeter.	250
Stockpiling soldering equipment.	251
Hoarding hand tools	253
Collecting cloths and cleansers	254
Loading up on lubricants	255
Stocking up on sticky stuff	256
Other tools and supplies	256
Stocking Up on Parts and Components	258
Solderless breadboards	258
Circuit-building starter kit.	259
Adding up the extras.	261
Organizing all your parts	262
Protecting You and Your Electronics	262
Understanding that electricity can really hurt.	262
Soldering safely	268
Avoiding static like the plague	268

CHAPTER 14: Interpreting Schematics 273

What's a Schematic and Why Should I Care?	274
Seeing the Big Picture	274
It's all about your connections.	275
Looking at a simple battery circuit	276
Recognizing Symbols of Power	277
Showing where the power is	277
Marking your ground	280
Labeling Circuit Components	281
Analog electronic components	283
Digital logic and IC components	285
Miscellaneous components	286
Knowing Where to Take Measurements	288
Exploring a Schematic.	288
Alternative Schematic Drawing Styles	290

CHAPTER 15: Building Circuits 293

Taking a Look at Solderless Breadboards	294
Exploring a solderless breadboard.	295
Sizing up solderless breadboard varieties.	297

Building Circuits with Solderless Breadboards	298
Preparing your parts and tools	298
Saving time with prestripped wires	299
Laying out your circuit	300
Avoiding damaged circuits	303
Soldering 101	304
Preparing to solder	304
Soldering for success	305
Inspecting the joint	306
Desoldering when necessary	307
Cooling after soldering	308
Practicing safe soldering	308
Creating a Permanent Circuit	309
Exploring a printed circuit board	309
Relocating your circuit to a perfboard	310
Making a custom circuit board	312
 CHAPTER 16: Mastering Your Multimeter to Measure Circuits	315
Multitasking with a Multimeter	316
It's a voltmeter!	317
It's an ammeter!	318
Ohm my! It's an ohmmeter, too!	318
Exploring Multimeters	319
Choosing a style: analog or digital	319
Taking a closer look at a digital multimeter	320
Homing in on the range	322
Setting Up Your Multimeter	324
Operating Your Multimeter	325
Measuring voltage	326
Measuring current	327
Measuring resistance	329
Running other multimeter tests	336
Using a Multimeter to Check Your Circuits	336
 CHAPTER 17: Putting Projects Together	339
Getting What You Need Right Off the Bat	340
Creating an LED Flasher Circuit	340
Exploring a 555 flasher	341
Building the LED flasher circuit	343
Checking your handiwork	345
Creating an LED Bike Flasher	346
Catching Intruders with a Light-Sensing Alarm	347
Assembling the light alarm parts list	349
Making your alarm work for you	350

Playing the C-Major Scale	350
Scaring Off the Bad Guys with a Siren	353
Scoping out the 555 siren parts list	354
How your warbler works	354
Building an Audio Amp with Volume Control	355
Creating Light Chasers	357
Building Light Chaser 1	358
Building Light Chaser 2	360
Red Light, Green Light, 1-2-3!	361
PART 4: THE PART OF TENS	365
CHAPTER 18: Ten Ways to Explore Electronics Further	367
Surfing for Circuits	367
Getting a Jumpstart with Hobby Kits	368
Simulating Circuit Operation	368
Scoping Out Signals	368
Counting Up Those Megahertz	369
Generating a Variety of Signals	369
Exploring Basic Computer Architectures	369
Microcontrolling Your Environment	370
Getting a Taste of Raspberry Pi	370
Try, Fry, and Try Again	371
CHAPTER 19: Ten Great Electronics Parts Sources	373
North America	373
All Electronics	374
Allied Electronics	374
Digi-Key	374
Electronic Goldmine	374
Jameco Electronics	375
Mouser Electronics	375
Parts Express	375
RadioShack	376
Outside North America	376
Premier Farnell (UK)	376
Maplin (UK)	376
What's RoHS Compliance?	377
New or Surplus?	377
GLOSSARY	379
INDEX	389