

Contents at a Glance

Introduction	1
Book 1: Getting Started with Electronics	7
CHAPTER 1: Welcome to Electronics	9
CHAPTER 2: Understanding Electricity	21
CHAPTER 3: Creating Your Mad-Scientist Lab	37
CHAPTER 4: Staying Safe	61
CHAPTER 5: Reading Schematic Diagrams	73
CHAPTER 6: Building Projects	87
CHAPTER 7: The Secrets of Successful Soldering	125
CHAPTER 8: Measuring Circuits with a Multimeter	137
CHAPTER 9: Catching Waves with an Oscilloscope	153
Book 2: Working with Basic Electronic Components	165
CHAPTER 1: Working with Basic Circuits	167
CHAPTER 2: Working with Resistors	207
CHAPTER 3: Working with Capacitors	239
CHAPTER 4: Working with Inductors	265
CHAPTER 5: Working with Diodes and LEDs	279
CHAPTER 6: Working with Transistors	305
Book 3: Working with Integrated Circuits	335
CHAPTER 1: Introducing Integrated Circuits	337
CHAPTER 2: The Fabulous 555 Timer Chip	349
CHAPTER 3: Working with Op-Amps	385
CHAPTER 4: Discovering Darlingtontons	405
Book 4: Beyond Direct Current	415
CHAPTER 1: Getting into Alternating Current	417
CHAPTER 2: Building Power Supplies	441
CHAPTER 3: Understanding Radio	453
CHAPTER 4: Working with Infrared	485
Book 5: Doing Digital Electronics	503
CHAPTER 1: Understanding Digital Electronics	505
CHAPTER 2: Getting Logical	521
CHAPTER 3: Working with Logic Circuits	541
CHAPTER 4: Working with Flip-Flops	577

Book 6: Working with Arduino Microprocessors	607
CHAPTER 1: Introducing Arduino	609
CHAPTER 2: Creating Arduino Sketches	625
CHAPTER 3: More Arduino Programming Tricks	657
CHAPTER 4: An Arduino Proximity Sensor	675
CHAPTER 5: Adding Sound and Motion to Your Arduino Projects	691
 Book 7: Hands-On Projects for Hobbyists	 723
CHAPTER 1: Building a Color Organ	725
CHAPTER 2: Crafting a Steampunk Crystal Radio	737
CHAPTER 3: Re-Creating a Retro Science-Fiction Robot Head	757
CHAPTER 4: Building an Infinity Life Box	769
 Index	 799

Table of Contents

INTRODUCTION	1
About This Book	2
Foolish Assumptions	4
Icons Used in This Book	5
Beyond the Book	5
Where to Go from Here	5
 BOOK 1: GETTING STARTED WITH ELECTRONICS	 7
CHAPTER 1: Welcome to Electronics	9
What Is Electricity?	10
But Really, What Is Electricity?	12
What Is Electronics?	15
What Can You Do with Electronics?	16
Making noise	16
Making light	17
Transmitting to the world	18
Computing	18
Looking inside Electronic Devices	18
 CHAPTER 2: Understanding Electricity	 21
Pondering the Wonder of Electricity	22
Looking for Electricity	23
Peering Inside Atoms	24
Examining the Elements	25
Minding Your Charges	26
Conductors and Insulators	27
Understanding Current	28
Understanding Voltage	30
Comparing Direct and Alternating Current	33
Understanding Power	35
 CHAPTER 3: Creating Your Mad-Scientist Lab	 37
Setting Up Your Mad-Scientist Lab	38
Equipping Your Mad-Scientist Lab	40
Basic hand tools	41
Magnifying glasses	43
Third hands and hobby vises	44
Soldering iron	46
Multimeter	47
Solderless breadboard	48

Wire	50
Batteries	52
Other things to stock up on	53
Stocking up on Basic Electronic Components	54
Resistors	54
Capacitors	55
Diodes	56
Light-emitting diodes	57
Transistors	57
Integrated circuits	58
One Last Thing	59
CHAPTER 4: Staying Safe	61
Facing the Realities of Electrical Dangers	62
Household electrical current can kill you!	62
Even relatively small voltages can hurt you	64
Sometimes voltage hides in unexpected places	66
Other Ways to Stay Safe	67
Keeping Safety Equipment on Hand	69
Protecting Your Stuff from Static Discharges	69
CHAPTER 5: Reading Schematic Diagrams	73
Introducing a Simple Schematic Diagram	74
Laying Out a Circuit	75
To Connect or Not to Connect	76
Looking at Commonly Used Symbols	77
Simplifying Ground and Power Connections	79
Labeling Components in a Schematic Diagram	82
Representing Integrated Circuits in a Schematic Diagram	84
CHAPTER 6: Building Projects	87
Looking at the Process of Building an Electronic Project	88
Envisioning Your Project	89
Designing Your Circuit	91
Prototyping Your Circuit on a Solderless Breadboard	96
Understanding how solderless breadboards work	97
Laying out your circuit	98
Assembling the coin-toss circuit on a solderless breadboard	100
What if it doesn't work?	106
Constructing Your Circuit on a Printed Circuit Board	107
Understanding how printed circuit boards work	107
Using a preprinted PCB	108
Building the coin-toss circuit on a PCB	110

	Finding an Enclosure for Your Circuit	115
	Working with a project box	117
	Mounting the coin-toss circuit in a box	118
CHAPTER 7:	The Secrets of Successful Soldering	125
	Understanding How Solder Works	126
	Procuring What You Need to Solder	127
	Buying a soldering iron	127
	Stocking up on solder	128
	Other goodies you need	129
	Preparing to Solder	130
	Soldering a Solid Solder Joint	131
	Checking Your Work	134
	Desoldering	135
CHAPTER 8:	Measuring Circuits with a Multimeter	137
	Looking at Multimeters	138
	What a Multimeter Measures	141
	Ammeter	141
	Voltmeter	142
	Ohmmeter	143
	Other measurements	144
	Schematic symbols for meter functions	144
	Using Your Multimeter	145
	Measuring current	147
	Measuring voltage	149
	Measuring resistance	150
CHAPTER 9:	Catching Waves with an Oscilloscope	153
	Understanding Oscilloscopes	154
	Examining Waveforms	156
	Calibrating an Oscilloscope	159
	Displaying Signals	161
	BOOK 2: WORKING WITH BASIC ELECTRONIC COMPONENTS	165
CHAPTER 1:	Working with Basic Circuits	167
	What Is a Circuit?	168
	Using Batteries	170
	Building a Lamp Circuit	173
	Project 1: A Simple Lamp Circuit	174
	Parts	174
	Steps	174

Working with Switches	175
The many ways to throw the switch	176
Making connections with poles and throws	177
Building a Switched Lamp Circuit	179
Project 2: A Lamp Controlled by a Switch	181
Parts	182
Steps	182
Understand Series and Parallel Circuits.	183
Building a Series Lamp Circuit.	185
Project 3: A Series Lamp Circuit.	185
Parts	186
Steps	186
Building a Parallel Lamp Circuit.	187
Project 4: A Parallel Lamp Circuit	188
Parts	189
Steps	189
Using Switches in Series and Parallel	190
Building a Series Switch Circuit	191
Project 5: A Series Switch Circuit.	192
Parts	192
Steps	193
Building a Parallel Switch Circuit.	193
Project 6: A Parallel Switch Circuit.	194
Parts	195
Steps	196
Switching between Two Lamps	197
Project 7: Controlling Two Lamps with One Switch	197
Parts	198
Steps	199
Building a Three-Way Lamp Switch.	200
Project 8: A Three-Way Light Switch	202
Parts	202
Steps	203
Reversing Polarity	203
Project 9: A Polarity-Reversing Circuit	204
Parts	205
Steps	205
CHAPTER 2: Working with Resistors	207
What Is Resistance?	208
Measuring Resistance	208
Looking at Ohm's Law	210

Introducing Resistors	211
Reading Resistor Color Codes	213
Reading a resistor's value	214
Understanding resistor tolerance	216
Understanding Resistor Power Ratings	217
Limiting Current with a Resistor	218
Project 10: Using a Current-Limiting Resistor	220
Parts	221
Steps	221
Combining Resistors	222
Combining resistors in series	223
Combining resistors in parallel	224
Mixing series and parallel resistors	226
Combining resistors in series and parallel	227
Project 11: Resistors in Series and Parallel	227
Parts	228
Steps	229
Dividing Voltage	232
Dividing Voltage with Resistors	233
Project 12: A Voltage Divider Circuit	233
Parts	234
Steps	235
Varying Resistance with a Potentiometer	236
CHAPTER 3: Working with Capacitors	239
What Is a Capacitor?	240
Counting Capacitance	243
Reading Capacitor Values	244
The Many Sizes and Shapes of Capacitors	246
Calculating Time Constants for Resistor/Capacitor Networks	249
Combining Capacitors	251
Combining capacitors in parallel	252
Connecting capacitors in series	252
Putting Capacitors to Work	254
Charging and Discharging a Capacitor	254
Project 13: Charging and Discharging a Capacitor	255
Parts	256
Steps	257
Blocking DC while Passing AC	258
Project 14: Blocking Direct Current	260
Parts	261
Steps	261

CHAPTER 4:	Working with Inductors	265
	What Is Magnetism?	266
	The north and south of magnetism	267
	Pondering permanent magnets	268
	Examining Electromagnets.	268
	Inducing Current	269
	Inductance and the art of resisting change	270
	Regarding henry	272
	Calculating RL Time Constants	273
	Calculating Inductive Reactance	275
	Combining Inductors	275
	Putting Inductors to Work	276
	Protecting Sensitive Circuits from Inductive Loads	278
CHAPTER 5:	Working with Diodes and LEDs	279
	What Is a Semiconductor?	280
	Doping: It's not just for athletes	282
	Understanding p-n junctions	284
	Introducing Diodes	285
	The Many Types of Diodes	287
	Rectifier diodes	287
	Signal diodes	288
	Zener diodes	289
	Using a Diode to Block Reverse Polarity	290
	Project 15: Blocking Reverse Polarity	291
	Parts	291
	Steps	292
	Putting Rectifiers to Work.	293
	Building Rectifier Circuits	295
	Project 16: Rectifier Circuits	296
	Parts	297
	Steps	297
	Introducing Light-Emitting Diodes	299
	Using LEDs to Detect Polarity	301
	Project 17: An LED Polarity Detector	302
	Parts	303
	Steps	303
CHAPTER 6:	Working with Transistors	305
	What's the Big Deal about Transistors?	306
	Why were transistors invented?	307
	Looking inside a transistor	308
	Examining transistor specifications	311
	Amplifying with a Transistor	312

Using a Transistor as a Switch	316
An LED Driver Circuit.	318
Project 18: A Transistor LED Driver.	319
Parts	320
Steps	321
Looking at a Simple NOT Gate Circuit	322
Building a NOT Gate	323
Project 19: A NOT Gate.	324
Parts	325
Steps	325
Oscillating with a Transistor.	327
Building an LED Flasher	329
Project 20: An LED Flasher	331
Parts	332
Steps	332
Wrapping Up Our Exploration of Discrete Components	334

BOOK 3: WORKING WITH INTEGRATED CIRCUITS 335

CHAPTER 1: Introducing Integrated Circuits 337

What Exactly Is an Integrated Circuit?	338
Looking at How Integrated Circuits Are Made	339
Integrated Circuit Packages	340
Using ICs in Schematic Diagrams	343
Powering ICs.	344
Avoiding Static and Heat Damage.	345
Reading IC Data Sheets.	346
Popular Integrated Circuits	347
555 timer.	347
741 and LM324 op-amp	348
78xx voltage regulator	348
74xx logic family	348

CHAPTER 2: The Fabulous 555 Timer Chip 349

Looking at How the 555 Works	349
Understanding 555 Modes.	352
Using the 555 in Monostable (One-Shot) Mode	352
Looking at a typical 555 monostable circuit	353
Looking at the resistor-capacitor circuit in a monostable timer	354
Calculating the time interval for a monostable circuit.	355
Using the 555 in Astable (Oscillator) Mode	356
Looking at a typical astable circuit	356
Controlling the time intervals in an astable 555 circuit	358
Calculating the duty cycle.	359

Using the 555 in Bistable (Flip-Flop) Mode	361
Using the 555 Timer Output	363
Doubling Up with the 556 Dual Timer	365
Making a One-Shot Timer	368
Project 21: A One-Shot 555 Timer Circuit	369
Parts	369
Steps	370
Making an LED Flasher	372
Project 22: An LED Flasher	373
Parts	374
Steps	375
Using a Set/Reset Switch	376
Project 23: An LED Flasher with a Set/Reset Switch	377
Parts	378
Steps	379
Making a Beeper	380
Project 24: An Audible Beeper	381
Parts	382
Steps	383
CHAPTER 3: Working with Op-Amps	385
Looking at Operational Amplifiers	386
Understanding Open Loop-Amplifiers	390
Looking at Closed Loop-Amplifiers	393
Using an Op-Amp as a Voltage Comparator	396
Working with the LM324 Op-Amp	399
Project 25: A Voltage Comparator	399
Parts	400
Steps	402
CHAPTER 4: Discovering Darlington's	405
Reviewing Transistor Gain	406
Looking at Darlington's	407
Examining the ULN2003 Darlington Array	409
Project 26: A High-Brightness LED Flasher	411
Parts	411
Steps	413
BOOK 4: BEYOND DIRECT CURRENT	415
CHAPTER 1: Getting into Alternating Current	417
What Is Alternating Current?	418
Measuring Alternating Current	420
Understanding Alternators	422
Understanding Motors	425

	Understanding Transformers	425
	Working with Line Voltage	428
	Using Line Voltage in Your Projects	429
	Being safe with line voltage	430
	Understanding hot, neutral, and ground.....	431
	Wires and Connectors for Working with Line Voltage.....	434
	Using Fuses to Protect Line-Voltage Circuits.....	436
	Using Relays to Control Line-Voltage Circuits	437
CHAPTER 2:	Building Power Supplies	441
	Using a Power Adapter.....	442
	Understanding What a Power Supply Does.....	443
	Transforming Voltage	444
	Turning AC into DC	445
	Half-wave rectifier	446
	Full-wave rectifier	447
	Bridge rectifier	447
	Filtering Rectified Current	448
	Regulating Voltage.....	450
CHAPTER 3:	Understanding Radio	453
	Understanding Radio Waves	454
	Transmitting and Receiving Radio.....	457
	Understanding radio transmitters	457
	Understanding radio receivers	458
	Understanding AM Radio	461
	Understanding FM Radio	463
	Tackling the Tuner.....	466
	Rolling Your Own Coil	468
	Choosing a Tuning Capacitor.....	471
	Considering a Simple AM Receiver Circuit.....	472
	Receiving Radio with a Single Chip	475
	Project 27: Building a Simple AM Radio Receiver	478
	Parts	479
	Steps	480
CHAPTER 4:	Working with Infrared	485
	Introducing Infrared Light	485
	Detecting Infrared Light	487
	Project 28: A Simple IR Detector	489
	Parts	490
	Steps	490
	Creating Infrared Light	491

Building a Proximity Detector	493
Building a Common-Emitter Proximity Detector	493
Project 29: A Common-Emitter Proximity Detector	495
Parts	496
Steps	496
Building a Common-Collector Proximity Detector	497
Project 30: A Common-Collector Proximity Detector	499
Parts	500
Steps	500
BOOK 5: DOING DIGITAL ELECTRONICS	503
CHAPTER 1: Understanding Digital Electronics	505
Distinguishing Analog and Digital Electronics	506
Understanding Binary	508
Knowing your number systems	508
Counting by ones	508
Doing the logic thing	511
Using Switches to Build Gates	513
Project 31: A Simple AND Circuit	515
Parts	515
Steps	516
Project 32: A Simple OR Circuit	517
Parts	517
Steps	518
Project 33: A Simple XOR Circuit	519
Parts	520
Steps	520
CHAPTER 2: Getting Logical	521
Introducing Boolean Logic and Logic Gates	522
Looking at NOT Gates	523
Looking at AND Gates	524
Looking at OR Gates	527
Looking at NAND Gates	529
Looking at NOR Gates	530
Looking at XOR and XNOR Gates	532
De Marvelous De Morgan's Theorem	534
All You Need Is NAND (Or NOR)	536
Universal NAND gates	537
Universal NOR gates	538
Using Software to Practice with Gates	539

CHAPTER 3:	Working with Logic Circuits	541
	Creating Logic Gates with Transistors	541
	Project 34: A Transistor NOT Gate	543
	Parts	545
	Steps	545
	A transistor AND gate circuit	546
	A transistor NAND gate circuit	547
	Project 35: A Transistor NAND Gate	548
	Parts	550
	Steps	550
	A transistor OR gate circuit	552
	A transistor NOR gate circuit	552
	Project 36: A Transistor NOR Gate	554
	Parts	555
	Steps	555
	Introducing Integrated Circuit Logic Gates	557
	Introducing the Versatile 4000-Series Logic Gates	560
	Building Projects with the 4011 Quad Two-Input NAND Gate	561
	Project 37: A CMOS NAND Gate	563
	Parts	564
	Steps	565
	Project 38: A CMOS AND Gate	566
	Parts	568
	Steps	568
	Project 39: A CMOS OR Gate	569
	Parts	571
	Steps	571
	Project 40: A CMOS NOR Gate	573
	Parts	574
	Steps	575
CHAPTER 4:	Working with Flip-Flops	577
	Looking at Latches	578
	Project 41: An Active-High Latch	582
	Parts	583
	Steps	583
	Project 42: An Active-Low Latch	585
	Parts	587
	Steps	587
	Looking at Gated Latches	589
	Project 43: A Gated D Latch	591
	Parts	592
	Steps	593

Introducing Flip-Flops	595
Project 44: A D Flip-Flop	599
Parts	600
Steps	600
Project 45: A Toggle Flip-Flop	602
Parts	603
Steps	603
Debouncing a CLOCK Input	605

BOOK 6: WORKING WITH ARDUINO MICROPROCESSORS

CHAPTER 1: Introducing Arduino	609
Introducing the Arduino UNO	609
Buying an UNO Starter Kit	613
Installing the Arduino IDE	613
Connecting to an UNO	614
Looking at a Simple Arduino Sketch	615
Running the Blink Program	617
Using a Digital I/O Pin to Control an LED	618
Project 46: Blinking an LED with an Arduino UNO	622
Parts	622
Steps	623
CHAPTER 2: Creating Arduino Sketches	625
Introducing C	626
Working with a Prototyping Shield	629
Building a Test Circuit	631
Project 47: An Arduino LED Test Circuit	632
Parts	633
Steps	633
Flashing the LEDs	635
Using Comments	637
Creating Identifiers	639
Using Variables	639
Doing Math	641
A Program That Uses Variables and Math	642
Using If Statements	644
Using While Loops	648
Using For Loops	651
Crafting Your Own Functions	654

CHAPTER 3:	More Arduino Programming Tricks	657
	Using a Push Button with an Arduino	657
	Checking the Status of a Switch in Arduino	659
	Project 48: A Push-Button Controlled Arduino LED Flasher	662
	Parts	663
	Steps	664
	Randomizing Your Programs	665
	Reading a Value from a Potentiometer	668
	Project 49: A Variable-Rate LED Flasher	671
	Parts	672
	Steps	672
CHAPTER 4:	An Arduino Proximity Sensor	675
	Using an Ultrasonic Range Finder	675
	Looking at the HC-SR04 Range Finder	676
	Generating a trigger pulse	677
	Reading pulse input	678
	Doing the math	678
	Using an LCD	679
	Connecting an LCD to Arduino	680
	Programming the LCD	681
	Building a Proximity Sensor	683
	Project 50: An Arduino Proximity Sensor	684
	Parts	685
	Steps	686
CHAPTER 5:	Adding Sound and Motion to Your Arduino Projects	691
	Using a Speaker with an Arduino	691
	Using the tone function	693
	Connecting a speaker to an Arduino	694
	Project 51: Creating Sound with a Speaker	696
	Parts	697
	Steps	697
	Sounding the alarm with Morse code	698
	Playing a siren	701
	Playing a song	702
	Using an MP3 Shield	705
	Assembling the Music Maker shield	706
	Preparing the micro-SD card	707
	Programming the Music Maker shield	707
	Building an Arduino Music Player	710

Project 52: Using a Music Maker Shield to Play Sounds	711
Parts	711
Steps	711
Using a Servo with an Arduino	713
Connecting a servo to an Arduino.	713
Programming a servo	715
Building a servo project	718
Project 53: Using a Servo with an Arduino.	718
Parts	720
Steps	720
BOOK 7: HANDS-ON PROJECTS FOR HOBBYISTS	723
CHAPTER 1: Building a Color Organ	725
Examining the Color Organ Project	726
Understanding How the Color Organ Works.	728
Getting What You Need to Build the Color Organ	729
Assembling the Color Organ	729
Using the Color Organ	735
CHAPTER 2: Crafting a Steampunk Crystal Radio	737
Considering the Crystal Radio Circuit.	739
Going Full Steampunk.	741
Cabinet	742
Coil assembly	743
Tuning capacitor assembly.	747
Diode detector	748
Terminals	750
Putting it together	751
Using the Steampunk Crystal Radio	753
Stringing up an antenna	753
Connecting to ground	754
Listening to the radio	755
CHAPTER 3: Re-Creating a Retro Science-Fiction Robot Head	757
Looking to Robby and B-9 For Inspiration	758
Conceiving VIN-e	760
Introducing VIN-e 1.0	761
The dome	762
The base	762
The central pillar	762
The eyes and nose.	763

The mouth	763
The “vacuum tubes”	764
The antenna	765
Looking at VIN-e’s Electronics	765
A Final Word about Safety	767
CHAPTER 4: Building an Infinity Life Box	769
Checking Out the Infinity Life Box.....	770
Looking at Mirrors.....	772
To Infinity and Beyond!.....	773
Playing Life	774
Shining Light on the LED Array	778
Soldering in the Upside Down.....	781
Building the Distribution Board.....	783
Constructing the Control Panel.....	785
Putting It All Together	786
Programming the MAX7219.....	792
Sketching the Infinity Life Box	794
INDEX.....	799

