

Index

Numbers

1:1 transformer, 151
60/40 rosin core, of solder, 252
555 timer
 in circuit builder starter kit, 260
 description of, 213
 light chaser projects, 357–360
 light-sensing alarm project, 347
 siren project, 354
 traffic signal project, 361–364
4017 decade counter
 in circuit builder starter kit, 260
 description of, 220–221
 disable pin in, 221
 light chaser projects, 357–360
 traffic signal project, 361–364

A

ABS plastic boxes, 257
AC (alternating current)
 adapters, 232–235
 blocking using inductors, 146
 capacitors to pass, 119
 coupling, 120
 current direction reversals in, 40
 defined, 19, 262
 electromagnetic induction of, 140
 function generator for, 369
 in inductor circuits, 143
 motors, 146
 not recommended for circuits, 232
 overview, 19–21
 rectification of, 163
 on schematics, 277–278
 speaker resistance to, 241
accelerometers, 238
acid-flux solder, 268

acoustic energy, 236
active (transistor partially on) mode, 179
A/D (analog-to-digital) converter, 222
adhesives, 256
air, as inductor core, 147
air dielectric, 127
air-core transformer, 283, 284
alarms
 alarm clocks, 120
 light-sensing, creating, 347–350
alkaline batteries, 230
All Electronics (retailer), 374
Allied Electronics (retailer), 374
alligator clips
 building LED circuit using, 42–43
 in capacitor discharging example, 115
 in circuit builder starter kit, 261
 needed for experiments, 32
 for soldering, 304, 306
alternating current (AC)
 adapters, 232–235
 blocking using inductors, 146
 capacitors to pass, 119
 coupling, 120
 current direction reversals in, 40
 defined, 19, 262
 electromagnetic induction of, 140
 function generator for, 369
 in inductor circuits, 143
 motors, 146
 not recommended for circuits, 232
 overview, 19–21
 rectification of, 163
 on schematics, 277–278
 speaker resistance to, 241
aluminum electrolytic dielectric materials, 123
ammeter, 288, 318
amperes (amps), 12

- amp-hour rating for batteries, 59, 229
- amplifiers
 - building, 355
 - common-emitter, 183
 - operational, 211–212, 284
- analog electrical signals, 181
- analog integrated circuits (ICs), 193
- analog-to-digital (A/D) converter, 222
- AND gate, 197
- anode, 22, 158
- antenna, 238
- antistatic ESD (electrostatic discharge) spray, 262
- antistatic wrist strap, 29, 257, 269–270, 304
- application notes, on datasheets, 206
- architectures, computer, 369–370
- Arduino microcontroller system, 370
- artist brushes, 255
- artwork, 274. *See also* schematics
- astable multivibrator
 - 555 timer as, 213–216
 - in LED flasher project, 341
 - in siren project, 354
- atoms, electrical charge of, 9–11
- audible frequency range, 241
- audio transistors, 186
- automobile audio systems, 120
- auto-ranging feature, in multimeter, 320, 322
- axial leads, in capacitors, 124

B

- back voltage, 141
- band-pass filters, 145
- bands, on resistors, 82
- band-stop (band-rejection) filters, 145, 149
- bandwidth, 211
- base 2 system, 194–195
- base 10 system, 194–195
- base current (I_B), 123
- base-emitter junction, in NPN transistor, 179
- BASIC Stamp microcontroller, 370
- batteries
 - alkaline, 230
 - amp-hour rating for, 59, 229

- capacitors compared to, 112–115
- cell in, 20
- in circuit builder starter kit, 260
- circuit symbols for, 23
- current supplied by, 101
- direct current from, 19–20
- disposable, 230
- lantern, 228
- lithium, 230
- need for experiments, 34
- non-rechargeable, 230
- potential dangers of, 267
- rechargeable, 230–231
- schematics of, 278
- transistor, 228
- types of, 229–231

- battery clips, 35, 229–230, 261
- battery holders, 230
- biasing
 - diodes, 160
 - transistors, 179, 181, 236
 - voltage, 159–160
- bike flasher, LED, creating, 346–347
- binary system, 181, 193–194
- bipolar junction transistors (BJTs), 172–174, 236
- bipolar transistors
 - for circuit projects, 187–188
 - in Darlington pair, 183
 - defined, 173
 - how they work, 178
 - identifying, 176, 186
 - overview, 173
 - phototransistor as, 236
 - testing, 333–334
- bistable multivibrator, 217
- bits (binary digits), 181, 194–195, 201
- BJTs (bipolar junction transistors), 172–174, 236
- bleeder jumper, to discharge capacitors, 332
- blown fuses, 319
- boxes, 257
- breadboard, solderless
 - building LED circuit using, 43–44
 - center gap on, 295
 - contact holes on, 296

- contact strips on, 297
- damage avoiding, 303
- defined, 204
- features of, 295
- internal electrical connections on, 326
- jumper wires for, 261
- laying out circuits on, 300–303
- overview, 28, 258
- parts and tools for, 298–299
- photo of, 294
- power rails on, 295–296, 301
- prestripped wire for, 299–300
- project ideas for, 340
- storage of, 297
- terminal strips on, 295
- using, 35–36, 294–297
- varieties of, 297
- breathing, difficulty with, 264
- break, in schematics, 275
- breakdown voltage, 164
- bridge, in schematics, 275
- bulb-style pump, 308
- buzzers, 241–242
- byte, defined, 196

C

- CA (cyanoacrylate) glue, 256
- cable
 - defined, 226
 - ribbon, 227
 - testing, 334–335
- cable ties, 257
- calculators, 24, 29
- calibrating, 325
- cameras, capacitors in, 120
- capacitance, 121–122, 302
- capacitive coupling, 120
- capacitors
 - batteries compared to, 112–113
 - charging and discharging, 113–120, 133–136
 - in circuit builder starter kit, 259–261
 - coupling, 120
 - defined, 112
 - dielectric types for, 123
 - electrolytic, 123
 - fully charged, 114
 - high-precision, 121
 - inductors compared to, 144
 - inductors with, 137
 - mica capacitors, 123
 - multimeter to test, 331–332
 - needed for experiments, 33
 - paper capacitors, 124
 - in parallel, 128–129
 - polarity of, 124
 - polarized, symbol for, 283
 - purpose of, 120–121
 - radial leads in, 124
 - reference ID for, 282
 - in series, 129–130
 - shapes and sizes of, 124
 - smoothing, 121
 - static shocks from, 269–270
 - to store electrical energy, 27, 113
 - symbol for, 128, 283
 - testing, 332
 - values of, 125–127
 - variable, 127, 283
 - variance among, 123
 - watching charge, 115–118
 - working voltage for, 123
- cardio-pulmonary resuscitation (CPR), 267
- cathode, 22, 158
- cell, in battery, 20
- cell phones, 21
- center gap, on solderless breadboard, 295
- ceramic dielectric materials, 122–123
- ceramic resonators, 150
- changeover switch, 62
- changing readings, detecting, 320
- charge, electric, 12
- charging capacitors, 113, 131
- chassis ground, 280
- cheat sheet, 3
- chemical energy, 49
- chip, 192. *See also* integrated circuits (ICs)

- chip assembly, 202
- chip densities, 193
- chokes, 141, 146. *See also* inductors
- circuit board. *See* printed circuit boards (PCBs)
- circuit breadboard, 294. *See also* solderless breadboard
- circuit builder starter kit, 259–261
- circuit diagram. *See* schematics
- circuit simulator, 368
- circuits. *See also* ground
 - AC, 41
 - batteries connected to, 228–230
 - combination circuits, creating, 62–65
 - constructing, soldering for, 308. *See also* solderless breadboard
 - integrated (ICs)
 - 555 timer as, 213–220
 - 4017 decade counter as, 220–221
 - analog, 193
 - categories of, 193
 - clocking notch on, 344
 - containing logic gates, 369
 - datasheets on, 207
 - defined, 176
 - digital, 193–194
 - electrostatic discharge (ESD) sensitivity of, 270
 - microcontrollers as, 221–222
 - mixed signal, 194
 - operational amplifiers as, 211–212
 - overview, 191
 - packaging for, 202, 205
 - part numbers to identify, 202
 - pinouts of, 207
 - purpose of, 192
 - on schematics, 285–286
 - on solderless breadboard, 258
 - specifications for, 202
 - transistors in, 176
 - working with, 222
 - for LED flasher project, 343
 - open circuits
 - inductor as, 143
 - overview, 38–39
 - transistor as, 184
 - overview, 17–18
 - projects on
 - logic gates, 209
 - transistors, 187
 - shape of, 67–69
 - short circuits
 - defined, 39, 143
 - inductors in, 142–143
 - ohmmeter to test for, 334
 - using inductors in, 146–147
- cladding, of printed circuit boards, 313
- cleansers, 254
- climate, 249
- clips
 - alligator clips
 - building LED circuit using, 42–43
 - in capacitor discharging example, 115
 - in circuit builder starter kit, 261
 - needed for experiments, 32
 - for soldering, 304, 306
 - battery clips, 35, 229–230, 261
 - wire clips, 257
- clock signals, 201
- clocking notch, on integrated circuits, 344
- closed position, of switches, 59
- cloths, 254–255
- CMOS (complementary metal-oxide semiconductor), 207, 303, 310
- coils, 152. *See also* inductors
- cold solder joint, 307
- collector current (I_C), 123
- color coding, 84
- combination circuit, creating, 62–65
- combined resistances, measuring, 93
- common ground, 48, 277, 280
- common-emitter amplifier, 183
- commutator, in DC motors, 243
- complementary metal-oxide semiconductor (CMOS), 207, 303, 310
- components. *See* electronic components
- compressed air, 254
- computer architectures, 369–370
- computers, electronic components in, 24
- condenser microphones, 34, 127, 236

- conductive path, 17–18
- conductors
 - overview, 12
 - resistance of, 74–75
 - wire form of, 15
- connections
 - parallel connections
 - capacitors in, 128–129
 - for multimeter, 325
 - overview, 56
 - resistors in, 91–94, 106–107
- on schematics, 274
- series connections
 - capacitors in, 129–130
 - for multimeter, 325
 - overview, 54–56
 - resistors in, 89–91
- on solderless breadboard, 301
- connectors, 226–227
- conservation of energy law, 18
- contact cleaner, 255
- contact holes, on solderless breadboard, 258, 294, 296–297
- contactless sensors, 146
- continuity tests, 318
- conventional current, 40–41, 158, 276
- converters
 - analog-to-digital (A/D), 222
 - digital-to-analog (D/A), 222
 - power converters, 21
- cooling, after soldering, 308
- cotton swabs, 255
- coulomb, 13
- coupling capacitor, 120
- covalent bond, in crystals, 156
- CPR (cardio-pulmonary resuscitation), 267
- cross-reference book, 161
- cross-sectional area, resistance and, 74
- crystal microphone, 236
- crystals
 - atoms in, 156
 - overview, 150
 - piezoelectric effect and, 150
 - reference ID for, 282

- resonance of, 150
 - symbol for, 284
- current
 - amplifying, 186–188
 - conventional, 40–41, 276
 - defined, 11
 - forward, 166
 - leakage, 119
 - limiting, 76–78, 342
 - magnetism to induce, 140
 - measuring, 12, 49–50, 327–328
 - overview, 9
 - real electron flow compared to, 20
 - reverse, 159
 - rheostat handling of, 86
 - sink, 207
 - smoothing out, using inductors for, 146
 - source, 207
 - strength of, 12
- current rating of diodes, 161
- cuticle sticks, 255
- cutoff (transistor off) mode, 179
- cutters, 253
- cyanoacrylate (CA) glue, 256

D

- Darlington pair of transistors, 183
- data bits, as information carriers, 196
- data communication systems, 25
- datasheets, 206–207
- DC (direct current)
 - from batteries, 19–20
 - defined, 19, 262
 - motors, 243–244
 - overview, 19
 - potential dangers of, 267
 - on schematics, 278
 - symbols for, 278
- decibel level, 242
- decimal system, 194, 196
- degreaser, 255
- DeGunther, Rik (*Solar Power Your Home For Dummies 2nd Edition*), 22

- desoldering, 307
- desoldering pump, 307
- diagonal cutters, 253
- dial pots, 85
- diaphragm, 236, 241
- dielectrics
 - air, 127
 - in capacitor testing, 332
 - as insulators, 112
 - types of, 122–123
- differential amplifier, 211
- Digi-Key (retailer), 374
- digital circuits, 193–194
- digital format, 181
- digital integrated circuits, 193–194
- digital logic, 193–194
- digital-to-analog (D/A) converter, 222
- dimers, 8, 67
- diodes
 - biasing, 159–160
 - conducting current through, 160
 - current rating of, 161
 - current restricted by, 27
 - defined, 158
 - forward-biased
 - light energy release in, 165–170
 - by multimeter, 162
 - junction, 158–161
- LEDs (light-emitting diodes)
 - circuit, building, 42–44
 - in circuit builder starter kit, 260
 - circuit diagram for, 76
 - for circuit projects, 170
 - forward-biased, 165–170
 - LED bike flasher, 346–347
 - LED flasher circuit, 340–346
 - light chaser projects, 357–360
 - needed for experiments, 33
 - reference ID for, 282
 - symbol for, 42, 284
 - turning on, 167–170
- needed for experiments, 33
- photodiodes, 184, 232, 236, 284
- rectifier diodes, 163
- reference ID for, 282
- reverse-biasing, 162–164
 - on schematics, 283–284
- semiconductor, 161–162
- signal diode, 162–163
- standard, symbol for, 284
- unbiased, 160
- as variable capacitors, 127
- visible light-emitting diodes (visible LEDs), 165
- Zener diode
 - reverse biasing, 159
 - symbol for, 284
 - voltage regulated with, 164–165
- DIPs (dual in-line packages), 203
- direct current (DC)
 - from batteries, 19–20
 - defined, 19, 262
 - motors, 243–244
 - overview, 19
 - potential dangers of, 267
 - on schematics, 278
 - symbols for, 278
- direction of current, 40
- disable pin, in integrated circuits, 221
- discharging capacitors, 113, 131
- discrete components, in solderless breadboard, 258
- disposable batteries, 230
- dot at intersection of two lines, in schematics, 275
- double-pole, double-throw (DPDT) switch, 62, 287, 335
- double-pole, single-throw (DPST) switch, 62, 287, 335
- double-pole switch, 61
- double-sided foam tape, 256
- double-throw switch, 61
- DPDT (double-pole, double-throw) switch, 62, 287, 335
- DPST (double-pole, single-throw) switch, 62, 287, 335
- drain, in field-effect transistors, 174
- drill, electric, 257
- dual in-line packages (DIPs), 203
- dual-gate MOSFETs (metal-oxide-semiconductor FETs), 176
- Dummer, Geoffrey, 192
- dynamic microphone, 236

E

- earth ground, 48, 280
- Edison, Thomas, 15
- electric charge, 9, 11–12
- electric current. *See* current
- electric drill, 257
- electrical circuit. *See* circuits
- electrical cords, soldering and, 268
- electrical energy. *See also* current
 - dangers of, 262–267
 - light from, 15–16
 - overview, 9
 - sources of, 17, 20. *See also* batteries
- electrically neutral atoms, 11
- electricity, defined, 9
- electrochemical reaction, 19
- electrocution, 267
- electrolytic capacitors, 123
- electromagnetic induction, 140, 236
- electromagnetism, 138–139, 243. *See also* inductors
- electromotive force (EMF or E), 14
- electronic components
 - defined, 23
 - in devices, 23
 - discrete, 258
 - Joule's Law for, 109
 - on schematics, 281
 - solderless breadboard connections for, 301
 - values of, 282
- Electronic Goldmine (retailer), 374–375
- electronic keyboard, creating, 350–353
- electronic systems, 8–9
- electronics, defined, 8
- electronics cleanser, 254
- electrons
 - charge of, 11
 - electrical energy of, 15–16
 - mobilizing to create current, 12–13
 - overview, 9
 - valence, 156
- electrostatic discharge (ESD), 175, 269. *See also* static electricity
- electrostatic discharge (ESD) spray, 262
- EMF (electromotive force), 14

- energy
 - acoustic, 236
 - chemical, 49
 - conservation of energy law, 18
 - electrical. *See also* current
 - dangers of, 262–267
 - light from, 15–16
 - overview, 9
 - source of, 18–20. *See also* batteries
 - heat energy, 16
 - secondary sources of, 20
- epoxy cement, 256
- equivalent capacitance, 129
- equivalent resistance
 - of complex circuits, 105–107
 - overview, 88
 - of parallel resistors, 91–92
 - of series resistors, 89
- ergonomics, 249
- ESD (electrostatic discharge), 175, 269. *See also* static electricity
- ESD (electrostatic discharge) spray, 262
- Europe, schematic symbols in, 290
- European Union Restriction on Hazardous Substances (RoHS) regulations, 377
- expanded notation for numbers, 195
- experimenter's PC board, 310
- external load, 18

F

- Fairchild Semiconductor, 193
- Faraday, Michael, 15, 138
- farads, capacitance measured in, 122
- Farnell (Web site), 376
- ferrite, as inductor core, 147
- FET. *See* field-effect transistor (FET)
- fiber-optic microphone, 237
- field-effect transistor (FET)
 - CMOS technology for, 207
 - dual-gate, 176
 - electrostatic discharge (ESD), sensitivity of, 270
 - in integrated circuits, 175
 - overview, 174–175
- fillet of solder, 307

filtering, using inductors for, 146

filters

- band-pass, 145

- band-stop, 145, 149

- high-pass, 145

- inductors as, 147

- low-pass, 145

- types of, 145

first-aid charts, 267

fixed inductors, 147

fixed resistors

- categories of, 81

- color-coding of, 82–84

- determining value of, 82–84

- inserting in circuits, 82

- vs. variable, 80–85

flashing lights, 214, 341

flip-flop circuit, 217

floating ground, 48

flow of electrons. *See* current

flush cutter, 253

flux, for soldering, 252

flux lines, from magnetism, 138–139

foam tape, 256

force, 16, 138

forward current, 159

forward voltage, 159, 166

forward-bias, 159

forward-biased diodes

- light energy release in, 165–170

- by multimeter, 162

Franklin, Benjamin, 15, 48, 262

frequency

- of buzzer, 242

- overview, 20

- of quartz crystals, 150

- range of operational amplifiers, 211–212

- resonance, 148

- speaker range of, 241

frequency counter, 369

full-wave rectification, 163

fully charged capacitor, 114

function generator, 369

fuses

- in AC-powered circuits, 266

- blown, 319

- correct input for, 329

- ohmmeter to check, 318–319

- resistance measuring of, 334

- testing, 334

G

gain, voltage, 182–183

gates (logic gates)

- circuit project on, 209

- data processing with, 196–199

- defined, 196

- diodes for, 170

- in field-effect transistors, 174

- integrated circuits containing, 369

- in integrated circuits (ICs), 196–199

- on schematics, 285–286

- symbols for, 285

- truth tables for, 199–201

gauge, of wire, 225–226

gauze bandage, 254

gear head, in DC motors, 243

glue, 256

grease, synthetic, 255

ground

- chassis, 280

- common, 45, 48, 277, 280

- defined, 45

- earth, 48, 277, 280

- floating, 48

- multimeter receptacle for, 321

- reference, 45

- on schematics, 278–280

- on solderless breadboard rail, 301

- for tools, 269, 271

gull wing leads, 204

H

hack saw, 257

half-wave rectification, 163

- hand saws, 257
- hand tools, 28, 253
- HDMI (High-Definition Multimedia Interface) cable, 226–227
- heart fibrillation, 264
- heat dissipation, 143
- heat energy, 16
- heat sensors, 238
- heat sink, 88
- helping hands clamp, 254, 305
- Henry, Joseph, 142
- henrys, as inductance measure, 142
- hertz (Hz), 21
- high voltage warnings, 264
- High-Definition Multimedia Interface (HDMI) cable, 226–227
- high-load applications, 88
- high-pass filters, 145
- high-power transistors, 183
- high-precision resistors, 81
- hobby kits, 368
- hot-melt glue gun, 256
- humidity, 249
- Hz (hertz), 21

I

- I_B (base current), 123
- I_C (collector current), 123
- IC datasheets, 206
- I_{Cmax} (maximum collector current), 185
- icons used in this book, 3
- ICs (integrated circuits)
 - 555 timer as, 213–220
 - 4017 decade counter as, 220–221
 - analog, 193
 - categories of, 193
 - clocking notch on, 344
 - containing logic gates, 369
 - datasheets on, 207
 - defined, 176
 - digital, 193–194
 - electrostatic discharge (ESD) sensitivity of, 270
 - microcontrollers as, 221–222

- mixed signal, 194
- operational amplifiers as, 211–212
- overview, 191
- packaging for, 202, 205
- part numbers to identify, 202
- pinouts of, 207
- purpose of, 192
- on schematics, 285–286
- on solderless breadboard, 258
- specifications for, 202
- transistors in, 176
- working with, 222
- IDE (integrated development environment), 221
- I_E (emitter current), 123
- impedance
 - defined, 102
 - of speakers, 241
- induced current, 140
- inductance, 151
- induction motors, 146
- inductors (induction coil)
 - in circuits, 144, 146–149
 - defined, 137
 - overview, 137, 141–143
 - reference ID for, 282
 - symbol for, 283
 - in tuning circuits, 148–150
 - unshielded, 137, 151
 - uses for, 145–146
- infrared light
 - light-emitting diodes (IR LEDs), 165
 - overview, 23
 - presence or absence of, 237
- infrared temperature sensors, 239
- input transducers, 235, 238–239
- insulators
 - defined, 112
 - dielectrics as, 112
 - semiconductors as, 155–156
- integrated circuits (ICs)
 - 555 timer as, 213–220
 - 4017 decade counter as, 220–221
 - analog, 193

integrated circuits (*continued*)

- categories of, 193
 - clocking notch on, 344
 - containing logic gates, 369
 - datasheets on, 207
 - defined, 176
 - digital, 193–194
 - electrostatic discharge (ESD) sensitivity of, 270
 - microcontrollers as, 221–222
 - mixed signal, 194
 - operational amplifiers as, 211–212
 - overview, 191
 - packaging for, 202, 205
 - part numbers to identify, 202
 - pinouts of, 207
 - purpose of, 192
 - on schematics, 285–286
 - on solderless breadboard, 258
 - specifications for, 202
 - transistors in, 176
 - working with, 222
- integrated development environment (IDE), 221
- interconnect wires. *See* jumper wires
- inverter, as NOT gate
- description of, 197
 - truth table for, 199
- inverting amplifier, 211–212
- ions, 19
- isolation transformer, 152

J

- jacks, 226
- Jameco (retailer), 375
- JFETs (junction FETs), 174, 175
- joint, solder, 306–307, 319
- Joule's Law, 109–110
- jumper wires
 - in kits, 261
 - need for experiments, 28
 - prestripped, 299–300
 - purpose of, 299
- junction diode, 158–159
- junction FETs (JFETs), 174, 175

K

- keyboard, creating, 350–353
- Kilby, Jack, 192, 193
- kilohms, 75
- Kirchhoff's Voltage Law, 47

L

- lantern battery, 228
- layout, 274. *See also* schematics
- LCD (liquid crystal display), 24
- LDRs (light-dependent resistors), 236
- leads
 - axial, 124
 - base, 173
 - collector, 173
 - correct connections for, 290
 - emitter, 173
 - gull wing, 204
 - radial, 124
 - for switches, 42
- leaf switch, 60
- leakage current, 119
- LEDs (light-emitting diodes)
 - in circuit builder starter kit, 259
 - circuit diagram for, 76
 - for circuit projects, 43–44, 170
 - forward-biased, 165–167
 - LED bike flasher, 346–347
 - LED flasher circuit, 340–346
 - light chaser projects, 357–360
 - needed for experiments, 33
 - reference ID for, 281
 - symbol for, 42, 283–284
 - turning on, 167–170
- light, from electrical energy, 15
- light bulb circuit example, 41–49
- light chasers, creating, 357–360
- light machine oil, 255
- light-dependent resistors (LDRs), 236
- light-emitting diodes (LEDs)
 - in circuit builder starter kit, 259
 - circuit diagram for, 76

- for circuit projects, 43–44, 170
- forward-biased, 165–167
- LED bike flasher, 346–347
- LED flasher circuit, 340–346
- light chaser projects, 357–360
- needed for experiments, 33
- reference ID for, 281
- symbol for, 42, 283–284
- turning on, 167–170
- lightning, 13, 268
- light-sensing alarm, creating, 347–350
- light-sensitive devices, as sensors, 236
- linear (analog) integrated circuits (ICs), 193
- linear power supply, 163
- linear resistance tracks, 85
- liquid crystal display (LCD), 24
- lithium batteries, 230
- live circuit, 266, 268
- load
 - for electrical energy, 17
 - high-wattage resistors for, 88
 - voltmeter to measure, 317
 - Zener diode for, 164
- logic, digital
 - binary system for, 196
 - on schematics, 285–286
 - truth tables in, 199
- logic gates
 - circuit project on, 209
 - data processing with, 196–199
 - defined, 196
 - diodes for, 170
 - in field-effect transistors, 174
 - integrated circuits containing, 370
 - in integrated circuits (ICs), 196–199
 - on schematics, 285–286
 - symbols for, 285
 - truth tables for, 199
- logic probe, 327
- loop, in schematics, 275
- low-noise transistors, 186
- low-pass filters, 145
- Low-Power Schottky series of TTL, 203

- low-power transistors, 186
- low-static clothing, 271
- LPS lubricant, 255
- lubricants, 255

M

- magnetic field
 - electricity to produce, 138–141
 - inductor coils for
 - in circuits, 145
 - overview, 143
 - unshielded, 151
 - in inductors and transformers, 27
- magnetized screwdriver, 253
- magnets, 11, 138–139
- magnifying glass, 253
- Maplin (retailer), 376
- mat, antistatic, 271
- matrix mathematics, 94
- maximum collector current (I_{Cmax}), 185
- maximum collector-to-emitter voltage (V_{CEmax}), 185
- maximum range, of multimeter, 323
- medium-power transistors, 186
- megohms, 75
- metal detectors, 146
- metal-oxide-semiconductor field-effect transistors (MOSFETs)
 - dual-gate, 174
 - in integrated circuits, 175
- mica capacitors, 125
- mica dielectric materials, 123–124
- microcontrollers, 221, 310, 370
- microphones
 - condenser, 34, 127, 236
 - crystal, 236
 - dynamic, 236
 - fiber-optic, 237
- microprocessors, 194
- milliamps, 13, 40, 88
- millihenrys, 142
- mini pushbutton (momentary on, normally open)
 - switches, 32
- mixed signal integrated circuits, 194

- monostable multivibrator, 216
- Morse code, 181
- MOSFETs (metal-oxide-semiconductor field-effect transistors)
 - dual-gate, 174
 - in integrated circuits, 175
- motion detectors, 237
- motors, speed control for, 24
- Mouser Electronics retailer, 375
- multimeter
 - analog, 319–320
 - auto-ranging feature on, 320, 324
 - circuit checking, 337
 - costs of, 250–251, 319
 - current measurement, 329
 - digital, 319–323
 - digital display on, 321
 - function selector on, 321
 - measuring current using, 49–50, 327–329
 - measuring resistance using, 329–335
 - measuring voltage using, 45–49, 317, 325, 327–329
 - overview, 28, 318
 - photo of, 316
 - range of, 322–323
 - on schematics, 288
 - setting up, 324–325
 - test leads on, 250, 321
 - using as ammeter, 318
- multiple ground symbols, 280
- Multisym simulator, 368
- multivibrator
 - astable, 214–216, 341, 352
 - bistable, 217
 - monostable, 216
- mutual inductance, 151
- Mylar dielectric materials, 123–124

N

- nail files, 255
- NAND gate
 - description of, 196
 - in projects, 207–211
 - on schematics, 285
 - as universal gate, 199

- National Electrical Code, 225
- NC (normally closed) switch, 61
- N-channel MOSFET, symbol for, 283–284
- needle-nose pliers, 253, 294, 298
- negative temperature coefficient (NTC) thermistor, 238
- negative terminal, 20
- neutral, electrically, 11
- neutrons, 9
- new surplus merchandise, 374
- NO (normally open) switch, 61
- no ground symbol, 280
- Nobel Prize in Physics, 193
- non-inverting input, 211
- non-rechargeable batteries, 230
- NOR gate, 197, 284
- normally closed (NC) switch, 61
- normally open (NO) switch, 61
- NOT gate (inverter), 197
- notation for numbers, expanded, 195
- Noyce, Richard, 193
- NPN transistors
 - model of, 179
 - overview, 173
 - symbol for, 283–284
 - testing, 334
- NTC (negative temperature coefficient) thermistor, 238
- N-type semiconductors, 158
- numbers, notation for, 195

O

- ohm (Ω), defined, 75
- Ohm, Georg, 96
- ohmmeter, 288, 318–319
- Ohm's Law
 - circuit analysis by, 98–108
 - circuit design and alteration by, 107–109
 - electricity dangers, 265
 - for inductors, 137
 - Joule's Law with, 109–110
 - overview, 96–98
 - testing, 102–105
- online articles, 4

- op-amp
 - defined, 212
 - as linear integrated circuit, 211–212
 - symbol for, 283–284
- open circuits
 - inductor as, 143
 - overview, 38–39
 - transistor as, 184
- open position, of switches, 59
- operational amplifier (op-amp)
 - defined, 211
 - as linear integrated circuit, 211–212
 - symbol for, 283–284
- OR gate
 - description of, 196
 - NAND gates converted to, 209
 - truth tables for, 199
- Ørsted, Hans Christian, 138–139
- oscillators
 - astable multivibrator as, 214–216
 - crystals in, 150
 - defined, 150
- oscilloscope
 - defined, 327
 - fast-changing signals tested with, 327
 - obtaining, 368
- output transducer, 239
- overvoltage protection, diodes for, 170

P

- packaging, for integrated circuits, 202–206
- pads, on printed circuit boards, 313
- pain, from current, 264
- paper capacitor, 124
- parallel connections
 - capacitors in, 128
 - for multimeter, 325
 - overview, 56–58
 - resistors in, 90–93, 106–107
- parallel resistors, 106
- part numbers, on schematics, 282
- Parts Express (retailer), 375
- passive infrared (PIR) motion detector, 237

- path, conductive, 17–18
- PCBs. *See* printed circuit boards (PCBs)
- P-channel MOSFET, symbol for, 284
- peak current, 166
- peak inverse voltage (PIV), 159
- peak reverse voltage (PRV), 159
- pencil eraser, 255
- perforated board (perfboard), 309–312. *See also* printed circuit boards (PCBs)
- Phillips head screwdriver, 253
- photodiodes, 184, 232, 236, 284
- photographic bulb brush, 253
- photoresistors, 236, 283
- photovoltaic cell. *See* solar cell
- PICAXE microcontroller, 370
- picture elements (pixels), 24, 196
- piezoelectric crystal, 238
- piezoelectric effect
 - in crystal microphone, 236
 - in crystals, 150
 - defined, 150
- pin headers, 227
- pinouts, integrated circuit
 - correct connections for, 290
 - explanation of, 205–207
- PIR (passive infrared) motion detector, 237
- PIV (peak inverse voltage), 159
- pixels (picture elements), 24, 196
- plasma TV, 24
- plastic boxes, 257
- plastic clips, 257
- plates, capacitor, 114
- pliers, 253, 298, 303
- plugs, 226, 288
- pn-junction, of semiconductors, 157
- PNP transistors, 173, 284, 333
- polarity
 - of capacitors, 124, 332
 - on schematics, 278
 - of speakers, 240
- polarized capacitor, symbol for, 283
- polyester dielectric material, 123–124
- polypropylene dielectric material, 123–124
- polystyrene dielectric material, 123

- position sensors, 238
- positive temperature coefficient (PTC) thermistor, 238
- potential difference, 15, 47
- potential drop, 15, 47
- potentiometers (pots). *See also* rheostats
 - in circuit builder starter kit, 259
 - encasing, 257
 - inside of, 84
 - multimeter to test, 331–332
 - operation of, 85
 - packages of, 85
 - purpose of, 80, 84–85
 - symbol for, 283–284
 - testing, 330
- power
 - battery size for, 21
 - calculating, 50–51
 - defined, 16
 - Joule’s Law of, 110
 - maximum dissipation of, 185
 - on schematics, 274, 277
- power converters, 21
- power plant, 20–21
- power rails, on solderless breadboard, 295–296, 384
- power rating
 - of components, 50
 - of resistors, 87–88
 - of speakers, 240
 - of Zener diode, 164
- power supply, 266
- power transistor, 176
- precision screwdrivers, 253
- Premier Farnell retailer, 376
- preset pots, 85
- pressure sensors, 238
- prestripped jumper wires, 299–300
- primary coil, 151–153
- printed circuit boards (PCBs)
 - capacitors on, 124
 - composition of, 310
 - custom, 312–313
 - perfboards, 310–312
 - resistors on, 86

- solderless breadboard compared to, 258–259
- through-hole mounted DIPs for, 203–204
- varieties of, 309

protons, 9, 11

prototyping board, 294. *See also* solderless breadboard

PRV (peak reverse voltage), 159–162

PTC (positive temperature coefficient) thermistor, 238

P-type semiconductors, 158

pulse current, 166

pulse-width modulation, 244

pulsing, timing of, 342

pump, desoldering, 307

pushbutton switch, 61

push-to-break switch, 61

Q

Q (transistor symbol), 284

quad 2-input AND gate, 198

quad 2-input NAND gate, 203

quarks, in atoms, 11

quartz crystals, 150

R

R (symbol for resistor), 75, 284. *See also* resistance

radial leads, in capacitors, 124

radio-receiver systems

- capacitors in tuning circuits of, 121
- inductors for, 148–150

RadioShack (retailer), 376

rail, 274

Raspberry Pi, 370

RC circuits

- operation of, 131–132
- RC time constant for, 132–136
- timers created with, 132–136

real current, 21, 40

receptacles, 226

rechargeable batteries, 230–231

rectification (AC to DC conversion), 163

rectifier diodes, 163

reference direction of current, 41

- reference ID, on schematics, 282–284
- registers, storing bits in, 201
- regulated power supplies, 21
- relay, 61, 282
- remote-control devices, 23
- resist pattern, on printed circuit boards, 313
- resistance
 - combined, measuring, 92–93
 - of conductors, 75
 - cross-sectional area, resistance and, 74
 - defined, 74
 - equivalent resistance
 - of complex circuits, 105
 - overview, 91
 - of parallel resistors, 93–94
 - of series resistors, 93–94
 - fixed resistors for, 80
 - Joule's Law in, 110
 - linear resistance tracks, 85
 - multimeter to measure, 329–335
 - Ohm's Law of
 - circuit analysis by, 97–107
 - circuit design and alteration by, 107
 - overview, 96–98
 - R symbol for, 75
 - resistor combinations for, 93
 - rotary resistance tracks, 85
 - of speakers, 240
 - testing unpowered circuits for, 318
 - in thermistors, 238
- resistors. *See also* fixed resistors; potentiometers (pots)
 - combinations of, 88–94
 - current flow restricted by, 27
 - fixed, 260
 - human body as, 263–264
 - to limit current through LED, 342
 - limiting current using, 76–78
 - multimeter to test, 329, 331
 - needed for experiment, 31–34
 - power ratings for, 87–88
 - purpose of, 75

- reference ID for, 282
- role of, 42
- symbol for, 283–284
- testing, 329
- tolerance, 81
- resonance, 148–149
- reverse current, 159
- reverse voltage, 159
- reverse-bias (nonconducting), 159
- reverse-bias diodes, 162
- reversing switch, 62
- rheostats
 - recognizing, 86
 - symbol for, 80
- ribbon cable, 227
- RL circuits, inductors in, 148
- RL time constant, 144
- RLC circuits, 149
- rocker switch, 60
- RoHS (European Union Restriction on Hazardous Substances) regulations, 377
- rosin core of solder, 252
- rosin core of solder, 60/40, 28, 252, 304
- rosin flux remover, 252
- rotary resistance tracks, 85

S

- safety
 - of circuit builder starter kit, 259
 - of cloths and cleansers, 254–255
 - electricity dangers, 263–267
 - of hand tools, 253
 - of household electronics, 86
 - of lubricants, 255
 - in soldering process, 251, 258, 267–268, 308
 - static electricity, 270–271
 - of supplies, 256
 - in workshop placement, 249
- safety glasses, 256, 268–269, 304
- saturating transistors, 182
- saturation (transistor fully on) mode, 184
- saws, hand saws, 257

- schematics
 - alternative drawing styles for, 290
 - analog electronic components on, 283–285
 - defined, 274
 - digital logic components on, 285
 - example of, 289
 - integrated circuits on, 285–286
 - for light bulb circuit, 41
 - overview, 273–276
 - resistor tolerance on, 81
 - switches and relays on, 282
 - transducers on, 287
- screwdrivers, 253
- secondary coil, 151–153
- secondary energy sources, 20
- self-contained power supply, 266
- self-inductance, 151
- semiconductors
 - circuits with, 176
 - as conductors and insulators, 155
 - defined, 21
 - for integrated circuits (ICs), 193
 - junction diode with, 158–162
 - N-types and P-types, 158
 - rheostats replaced by, 86
 - for solar cells, 21
 - temperature sensors, 238
- sensors
 - defined, 24
 - description, 24
 - types of, 235–238
- series connections
 - for multimeter, 325
 - overview, 55–56
- shielded inductors, 146–147
- shielded wire, 227
- shock, electrical, 263
- short circuits
 - defined, 39, 143
 - inductors in, 142–143
 - ohmmeter to test for, 331–332
- signal
 - amplified by transistors, 180–182
 - clock, 201
 - function generator for, 369
 - switched by transistors, 183–184
- signal diode, 163
- signal ground, 280
- signal transistors, 176
- silver solder, 268
- single ground symbol, 280
- single-pole, double-throw (SPDT) switch, 31, 61, 64, 287, 335
- single-pole, single-throw (SPST) switch, 61, 62, 65, 287, 335
- single-pole switch, 61
- single-throw switch, 61
- sink current, 207
- siren project, 353–355
- slide pots, 85
- slide switch, 60
- small-outline integrated circuit (SOIC), 204
- smoothing capacitors, 121
- SMT (surface-mount technology), 87, 204
- sockets, 203
- SOIC (small-outline integrated circuit), 204
- solar cell
 - defined, 21
 - overview, 21
 - on schematics, 277
- solar panels, 232
- Solar Power Your Home For Dummies, 2nd Edition* (DeGunther), 22
- solder, 252, 268
- solder braid, 252, 307
- solder joint, 251
- solder sucker, 252, 307
- solder wick, 252, 307
- solderable breadboards. *See* perforated board (perfboard)
- soldering
 - cooling after, 308
 - defined, 251
 - equipment for, 251–253
 - process, 307–308
 - safety precautions, 251, 258, 267–268, 308
 - solder removal tools for, 252
- soldering irons, 28, 251, 268
- soldering pencil, 251

- soldering stand, 251
- soldering station, 251
- solderless breadboard
 - building LED circuit using, 42–43
 - center gap on, 295
 - contact holes on, 295–296
 - contact strips on, 297
 - damage avoiding, 303
 - defined, 204
 - features of, 295
 - internal electrical connections on, 326
 - jumper wires for, 261
 - laying out circuits on, 299–300
 - overview, 26, 258
 - parts and tools for, 298–299
 - photo of, 295
 - power rails on, 295–296, 301
 - prestripped wire for, 299–300
 - project ideas for, 339
 - storage of, 297
 - terminal strips on, 295
 - using, 35–36, 294–295
 - varieties of, 295
- solenoids, 141. *See also* inductors
- solid-core transformer, symbol for, 284
- solid wire, 224, 297
- solid-state electronics, 158
- source, in field-effect transistors (FETs), 175
- source current, 207
- source of electrical energy, 17, 20. *See also* batteries
- SPDT (single-pole, double-throw) switch, 31, 61, 64, 287, 335
- speakers, 240–241, 261
- specifications, for integrated circuits (ICs), 202
- speed, of DC motors, 242
- SPICE (Simulation Program with Integrated Circuit Emphasis) algorithm, 368
- split DC power, 278
- sponge, for use with soldering, 252
- spray-on synthetic lubricant, 255
- spring-loaded pump, 307
- SPST (single-pole, single-throw) switch, 61, 62, 65, 287, 335
- standard diode, symbol for, 284
- standard-precision resistors, 81
- static electricity
 - avoiding, 268–271
 - CMOS chip sensitivity to, 203
 - defined, 13
 - description, 13
 - dissipation of, 204
 - soldering generating, 310
- step-up/step-down transformers, 152–153
- stocking distributors, 374
- strain relief, 266
- stranded wire, 224, 299
- stray capacitance, 302
- strength of current, from solar cells, 21
- subatomic particles, 9
- super glue, 256
- superconductors, 74
- surface-mount technology (SMT), 87, 204, 309
- switches
 - in circuit builder starter kit, 259–261
 - controlling action of, 60–61
 - double-pole, double-throw (DPDT) switch, 62, 287, 335
 - double-pole, single-throw (DPST) switch, 62, 287, 335
 - multimeter to test, 334
 - on schematics, 286
 - single-pole, double-throw (SPDT) switch, 31, 61, 64, 287, 335
 - single-pole, single-throw (SPST) switch, 61, 62, 65, 287, 335
 - testing resistance of, 318
 - types of, 60–62
- switching, 60–62
- symbols, for power, 279–280
- synthetic grease, 255

T

- tantalum electrolytic dielectric material, 124
- temperature, resistance strength by, 74
- temperature sensors, 239
- terminal block, 226
- terminal strips, on solderless breadboard, 295
- terminals, 20, 86, 226

- test point (TP), 288
- testing
 - capacitors, 331–332
 - fuses, 335–336
 - Ohm’s Law, 103–104
 - potentiometers, 330
 - resistors, 329
 - transistors, 329
- Texas Instruments, Inc., 192–193
- thermistor
 - defined, 74
 - purpose of, 238
 - resistance behavior in, 74
- thermocouple, 239
- third hand clamp, 253, 305
- through-hole mounted DIPs, 203
- timer
 - capacitors for, 213–217
 - circuit builder starter kit, 259
 - LED flasher project, 340, 343
 - light bulb circuits, 8
 - light chaser projects, 357–360
 - light-sensing alarm project, 347
 - RC circuits for, 304
 - siren project, 353–355
 - traffic signal project, 361–362
- timing cycles, controlling, 79
- tingling sensation, from current, 265
- tip cleaner paste, 252
- tolerance
 - of capacitors, 126
 - of resistors, 81
- tone generator, 347
- tools, 252–253, 256–257. *See also names of specific tools*
- total power dissipation (P_{total}), 185
- trace
 - defined, 313
 - in printed circuit boards, 313, 319
- transducer, 235, 238, 239, 287
- transformers
 - 1:1 transformer, 152
 - air-core, 283
 - isolation transformer, 152
 - solid-core transformer, symbol for, 284
 - step-up/step-down transformers, 152–153
 - to store electrical energy, 27
 - transformer action, 151
 - unshielded inductors for, 147, 151
 - wall, 266
- transistors
 - amplifying signals with, 180–182
 - battery, 228
 - bipolar transistors
 - bipolar junction, 173–174, 236
 - for circuit projects, 186–190
 - in Darlington pair, 183
 - defined, 173
 - how they work, 178
 - identifying, 176, 186
 - overview, 173
 - phototransistor as, 236
 - testing, 329–330
 - for circuit projects, 189
 - Darlington pair of, 183
 - defined, 25
 - field-effect transistor (FET)
 - CMOS technology for, 203
 - dual-gate, 174
 - electrostatic discharge (ESD), sensitivity of, 269
 - in integrated circuits (ICs), 175
 - overview, 174–175
 - high-power, 186
 - how transistors work, 176–178
 - identifying, 176, 186–190
 - low-noise, 186
 - low-power, 186
 - medium-power, 186
 - model of, 180
 - modes
 - active, 77
 - cutoff, 179
 - saturation, 179
 - MOSFETs (metal-oxide-semiconductor field-effect transistors)
 - dual-gate, 174
 - in integrated circuits, 175

- multimeter to test, 329
- needed for experiments, 34
- NPN transistors
 - model of, 180
 - overview, 173
 - symbol for, 283–284
 - testing, 334
- operations of, 179
- overview, 27
- PNP transistors, 173, 284, 334
- power transistor, 176
- purpose of, 172
- ratings for, 185–186
- reference ID for, 282
- resistors to limit current to, 76
- saturating, 179
- switching signals with, 184
- testing, 329–330
- transistor action, 178
- using as amplifier, 179
- using as switch, 179
- transistor-transistor logic (TTL), 203
- trim pots, 85
- troubleshooting live circuits, 266
- truth tables, 199
- TTL (transistor-transistor logic), 203
- tuning circuits
 - inductors in, 144
 - overview, 121
 - resonance in, 150
- two-state representation, in binary system, 196

U

- unbiased diodes, 160
- uninterruptible power supplies (UPSs), 120, 170
- United Kingdom, schematic symbols in, 291
- universal gates, 199
- unpowered circuits, for testing, 318
- updates to this book, 4
- UPSs (uninterruptible power supplies), 120, 170

V

- V symbol (volts), 14
- vacuum tubes, 172
- valence electrons, 156
- varactors, 127
- variable capacitors, 127, 283
- variable coil, 146. *See also* inductors
- variable inductors, 146
- variable resistors. *See* potentiometers (pots); rheostats
- varicaps, 127
- V_{CEmax} (maximum collector-to-emitter voltage), 185
- visible light-emitting diodes (visible LEDs), 165
- voltage
 - across quartz crystals, 150
 - back, 141
 - batteries for, 46
 - from battery pack, measuring, 45
 - battery terminals for, 19
 - bias, 159–160
 - breakdown voltage, 164
 - of buzzer, 241
 - calculating, 107
 - capacitor, 114
 - of DC motors, 242
 - drop in
 - as alternative term, 15
 - calculating, 107
 - explanation of, 49
 - as force, 14, 16
 - forward voltage, 159, 166
 - gain in, 182–183
 - high voltage warnings, 264
 - magnetism to induce, 140–141
 - maximum collector-to-emitter voltage (V_{CEmax}), 185
 - measuring using multimeter, 45–49, 325, 327–329
 - Ohm's Law for, 97–98, 99–106
 - overview, 14–15
 - overvoltage protection, diodes for, 170
 - peak inverse voltage (PIV), 159
 - peak reverse voltage (PRV), 159–162

- voltage (*continued*)
 - reducing, 78–79
 - resistors to control, 80
 - reverse voltage, 159
 - rheostat handling of, 86
 - rise in, 47
 - on schematics, 277
 - warnings of, 264
 - working voltage, 114, 123
 - Zener diode to regulate, 164–165
- voltage divider
 - circuit as, 101
 - defined, 79
 - resistance as, 78
- voltmeter, 288, 317

W

- wall transformer, 266
- wall warts. *See* alternating current (AC) adapters
- water-based household cleaner, 254
- watts (W), 16
- waveform, on schematics, 279
- WD-40, 255
- Weller WES51 soldering iron, 271
- wetted sponge, to remove solder, 252
- white household glue, 256
- wiper, on multimeter, 330
- wire
 - in circuit builder starter kit, 259
 - gauge of, 225–226

- jumper, 299
- multimeter to test, 334
- need for experiments, 32
- prestripped, 299–300
- purchasing, 261
- securing, 266
- strain relief, 266
- types of, 224
- wrapping of, 225
- wire clips, 257
- wire cutters, 253
- wire stripper, 253, 298–300
- wooden boxes, 257
- work, electrical energy for, 23
- workbench, 249
- working voltage, 114, 123
- workshop, placement of, 248–249
- wrapping, wire, 225
- wrist strap, antistatic, 29, 257, 270–271, 304

X

- XNOR gate, 197
- XOR gate, 197

Z

- Zener diode
 - reverse biasing, 159
 - symbol for, 283–284
 - voltage regulated with, 164–165
- zigzag symbol, 42